

CSC 1301 – Spring 2020

Homework #1

Due 02/04/2020 11:59PM

Submission Requirements

You must turn work at the SPECIFIED TIME so you can receive credit for Homework!

*Homework 1 **must be submitted on icollege** by the due date and time. Late homework will be subject to a penalty, as stated in the course grading policy. No email or hard copies of homework will be accepted.*

*You may discuss the assignments with other students in the class, but (as stated in the academic honesty policy) your written answers **must be your own**, and you must list the names of other students you discussed the assignment with.*

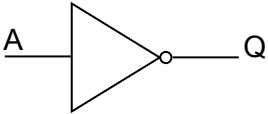
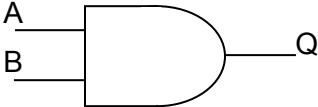
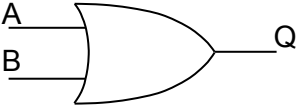
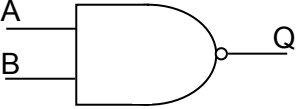
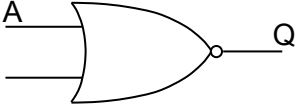

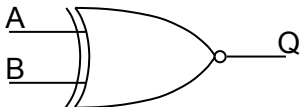
How to Submit

Log into **iCollege** ([iCollege](#)), select the class to view its drop box folders, select the correct folder for the given assignment and upload the file there.

You will get a confirmation email. Please save the conformation email in the event something goes wrong, for example work was submitted to the wrong folder etc...,

Feel free to hand draw the gates then use any Scanner app via mobile device such as CamScanner, Tiny Scanner just to name a few. These are a just a small scanner app that turns mobile device into a portable document scanner and scan everything as images or PDFs. Save file as PDF then upload to icollege.

The following table should remind you of the work we did in class


Gate	Symbol	Boolean Equation
NOT		$Q = \overline{A}$
AND		$Q = A.B$
OR		$Q = A + B$
NAND		$Q = \overline{A.B}$
NOR		$Q = \overline{A + B}$
EXOR		$Q = A \oplus B$ or $Q = \overline{A}.B + A.\overline{B}$
EXNOR		$Q = \overline{A \oplus B}$ or $Q = \overline{A}.B + A.\overline{B}$

Gates question 1 – 7 = [44 pts - 7 points each]

1. Draw an AND gate and list all the possible input values that will cause it to produce a value of 1.
2. Draw an OR gate and list all the possible input values that will cause it to produce a value of 1.
3. Draw an XOR gate and list all the possible input values that will cause it to produce a value of 1.
4. Draw a NOT gate and list all the possible input values that will cause it to produce a value of 1.


5. Draw and label the symbol for a TWO-input NOR gate, then show its behavior with a truth table.

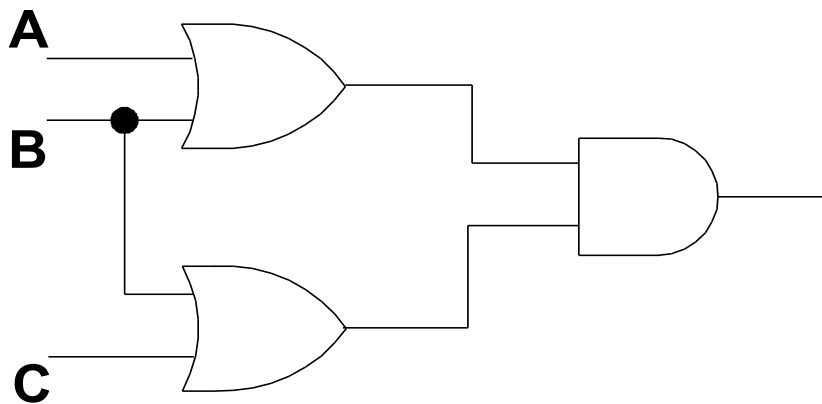6. Show the behavior of the following circuit with a truth table:



A	B	C

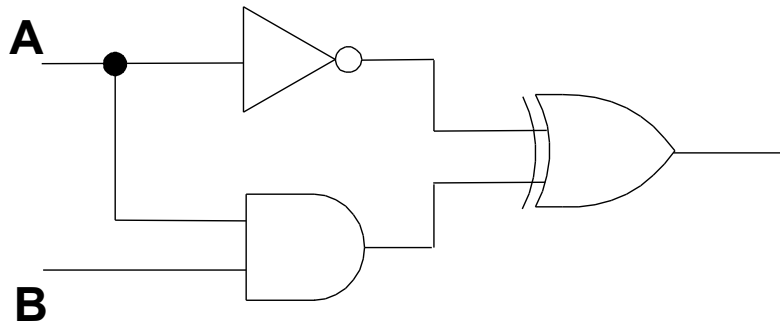
7. Show the behavior of the following circuit with a truth table:



A	B	Y

Questions 8 – 13 = [56 pts – 9.33 points each]

8. Complete the truth table for the following system. Hint**** $A'B + (B+C)'$

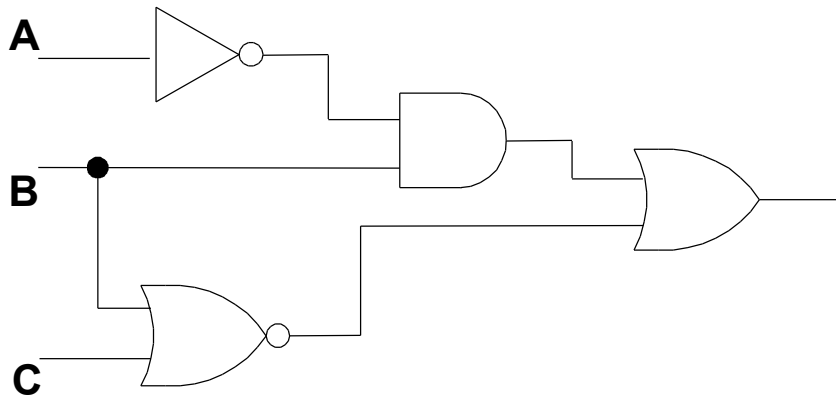[illegible]

10. Draw and label the symbol for a TWO-input NAND gate, then show its behavior with a truth table.

11. Draw a circuit diagram corresponding to the following Boolean expression:
 $(A + B)(B + C)$

12. Draw a circuit diagram corresponding to the following Boolean expression:
 $(AB)' + (CD)'$

13. Draw a circuit diagram corresponding to the following Boolean expression:
 $(AB + C)D$